

## **Lab #3 Example, Counter**

Sean Graham

Kennesaw State University

CPE 3020: VHDL Design with FPGAs

Professor Scott Tippens

Spring 2025

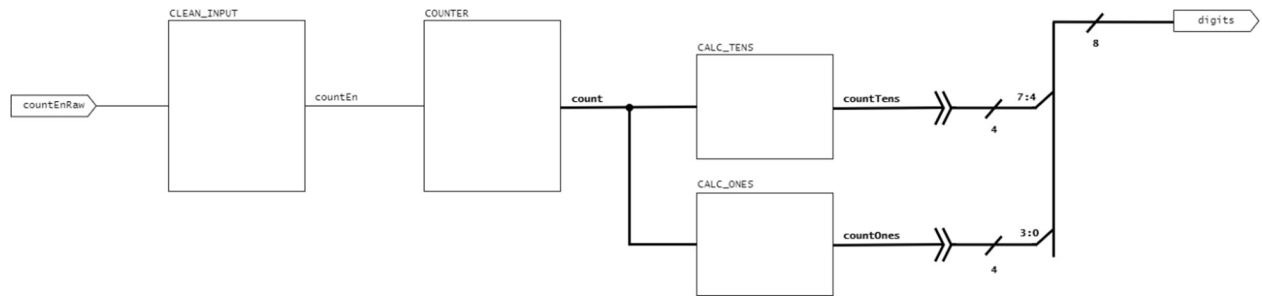


Fig. 1. Design diagram

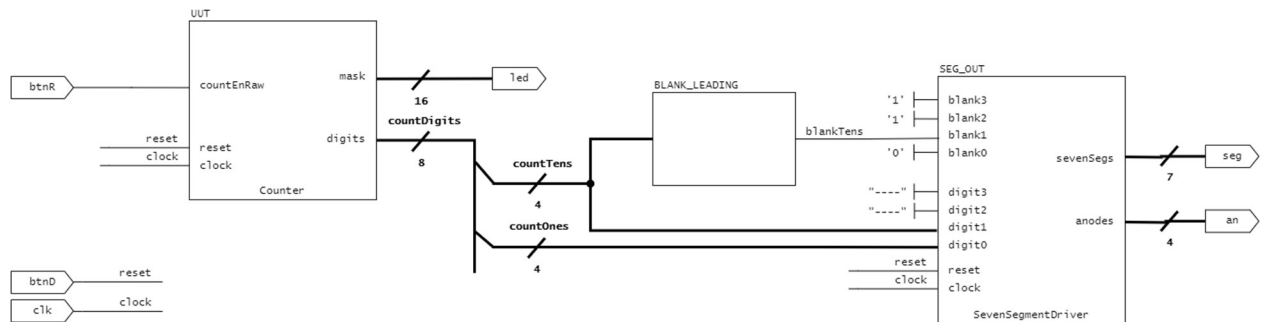


Fig. 2. Wrapper diagram

Note, SevenSegmentDriver is a component from the external package *physical\_io\_package*. Its diagrams and description have not been included.

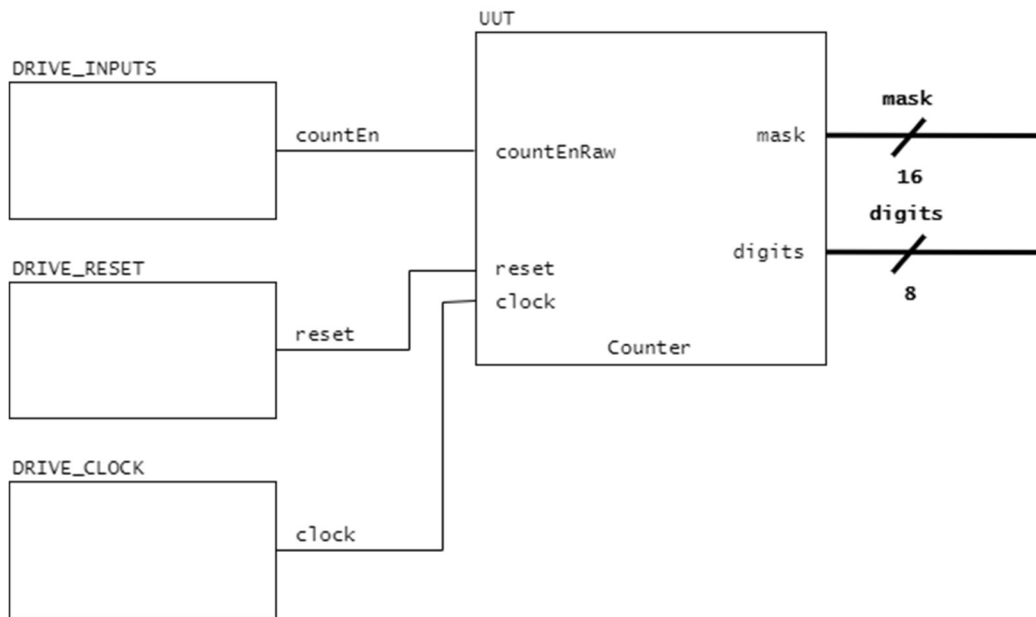


Fig. 3. Testbench diagram

 


Fig. 4. Simulation results, right direction

```

-----
--
-- Lab 03 Demo: Counter
-- Sean Graham
--
-- Simple 4-bit synchronous counter. On reset, count is cleared to 0.
-- Counts to 15 on countEn then overflows to 0 again.
--
-- Count is output as an 8-bit BCD string, countBits.
-- A 16-bit mask with the corresponding bit high is also output.
--
-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Counter is
    port(
        clock: in std_logic;
        reset: in std_logic;

        countEnRaw: in std_logic;

        digits: out std_logic_vector(7 downto 0); -- bcd tens (15:8), ones (7:0)
        mask: out std_logic_vector(15 downto 0)
    );
end Counter;

architecture Counter_ARCH of Counter is
    -----CONSTANTS-----
    constant ACTIVE: std_logic := '1';

    -- when a low input is followed by a high, signal has just gone high
    constant FIRST_ACTIVE: std_logic_vector(1 downto 0) := (ACTIVE, not ACTIVE);

    -----SIGNALS-----
    signal count: integer range 0 to 15;

    -- synchronized input
    signal countEn: std_logic;

    -- digits
    signal countTens: integer range 0 to 1;
    signal countOnes: integer range 0 to 9;
begin
    -- synchronize async button input and trigger on first cycle high
    -- note, physical_io_package has components for this
    CLEAN_INPUT: process (reset, clock) is
        -- in : countEnRaw
        -- out: countEn

        -- buffer of the last 4 inputs
        -- introduces a small delay for inputs to propagate
        variable inputs: std_logic_vector(3 downto 0);
    begin
        if (reset = ACTIVE) then
            -- on reset, saturate the buffer with low inputs
            countEn <= not ACTIVE;
            inputs := (others => not ACTIVE);
        elsif rising_edge(clock) then
            -- shift next input into buffer
            inputs := countEnRaw & inputs(3 downto 1);

            -- count only when the button is first pressed
            -- note, effectively shortens the synchronizer chain by 2
            if (inputs(1 downto 0) = FIRST_ACTIVE) then
                countEn <= ACTIVE;
            end if;
        end if;
    end process;
end Counter_ARCH;

```

```

-- store and update count
MAKE_COUNT: process (reset, clock) is
    -- in : countEn
    -- out: count
begin
    if (reset = ACTIVE) then
        -- reset to 0
        count <= 0;
    elsif rising_edge(clock) then
        -- increment on count
        if (countEn = ACTIVE) then
            if (count < 15) then
                count <= count + 1;
            else
                count <= 0;
            end if;
        end if;
    end if;
end process;

-- convert to decimal digits
CALC_TENS: countTens <= (count / 10);
CALC_ONES: countOnes <= (count mod 10);

-- merge and convert to bcd
BCD_TENS: digits(7 downto 4) <= std_logic_vector(to_unsigned(countTens, 4));
BCD_ONES: digits(3 downto 0) <= std_logic_vector(to_unsigned(countOnes, 4));

-- create mask pattern
MAKE_MASK: process (count) is
begin
    mask <= (others => not ACTIVE);
    mask(count) <= ACTIVE;
end process;
end Counter_ARCH;

```

```

-----
--
-- Lab 03 Demo: Counter_BASYS3
-- Sean Graham
--
-- wrapper implementing the Counter entity on the BASYS3 board.
--
-- when the right button is pressed, the counter increments.
-- when the down button is pressed, the counter is reset.
--
-- Current count is shown in decimal on the board's seven-segment display,
-- and the corresponding LED (count mod 16) is lit.
--
-----

library ieee;
use ieee.std_logic_1164.all;

entity Counter_BASYS3 is
    port(
        clk: in std_logic;

        btnR: in std_logic;
        btnD: in std_logic;

        led: out std_logic_vector(15 downto 0);
        seg: out std_logic_vector(6 downto 0);
        an: out std_logic_vector(3 downto 0)
    );
end Counter_BASYS3;

architecture Counter_BASYS3_ARCH of Counter_BASYS3 is
    -----CONSTANTS-----
    constant ACTIVE: std_logic := '1';

    -- bcd literals
    constant BCD_BLANK: std_logic_vector(3 downto 0) := "----";

    -----COMPONENTS-----
    -- uut: counter
    component Counter is
        port(
            clock: in std_logic;
            reset: in std_logic;

            countEnRaw: in std_logic;

            digits: out std_logic_vector(7 downto 0); -- bcd tens (15:8), ones (7:0)
            mask: out std_logic_vector(15 downto 0)
        );
    end component;

    -- seven segment driver
    component SevenSegmentDriver is
        port(
            reset: in std_logic;
            clock: in std_logic;

            digit3: in std_logic_vector(3 downto 0); --leftmost digit
            digit2: in std_logic_vector(3 downto 0); --2nd from left digit
            digit1: in std_logic_vector(3 downto 0); --3rd from left digit
            digit0: in std_logic_vector(3 downto 0); --rightmost digit

            blank3: in std_logic; --leftmost digit
            blank2: in std_logic; --2nd from left digit
            blank1: in std_logic; --3rd from left digit
            blank0: in std_logic; --rightmost digit

            sevenSegs: out std_logic_vector(6 downto 0); --MSB=g, LSB=a
            anodes: out std_logic_vector(3 downto 0) --MSB=leftmost digit
        );
    end component;

```

```

-----SIGNALS-----
-- asynchronous inputs
signal clock: std_logic;
signal reset: std_logic;

-- counter
signal countEn: std_logic;
signal countDigits: std_logic_vector(7 downto 0);

-- bcd digits
signal countTens: std_logic_vector(3 downto 0);
signal countOnes: std_logic_vector(3 downto 0);

-- seven seg
signal blankTens: std_logic;
begin
-- map async inputs
clock <= clk;
reset <= btnD;

-- map counter component
UUT: Counter port map(
    clock => clock,
    reset => reset,

    countEnRaw => btnR,

    digits => countDigits,
    mask => led -- drive led output
);

-- split BCD count into digits
countTens <= countDigits(7 downto 4);
countOnes <= countDigits(3 downto 0);

-- blank leading digit when it is zero
BLANK_LEADING: with countTens select
    blankTens <= (not ACTIVE) when "0000",
    ACTIVE      when others;

-- map seven segment component
SEG_OUT: SevenSegmentDriver port map(
    reset => reset,
    clock => clock,

    digit3 => BCD_BLANK, -- don't care, will be blanked
    digit2 => BCD_BLANK, -- don't care, will be blanked
    digit1 => countTens,
    digit0 => countOnes,

    blank3 => ACTIVE, -- always blanked
    blank2 => ACTIVE, -- always blanked
    blank1 => blankTens,
    blank0 => (not ACTIVE), -- always visible

    sevenSegs => seg,
    anodes => an
);
end Counter_BASYS3_ARCH;

```

```
-----
--
-- Lab 03 Demo: Counter_TB
-- Sean Graham
```

```
--
--     Testbench for the Counter entity.
--
--     Tests the first 16 states of the counter, at which point behavior is
--     expected to loop. For each check, increments the counter then checks
--     state.
--
--     Note, code written in the wrapper is *not* tested by the testbench.
--     so you want to keep as much logic as reasonable in the UUT.
--
-----
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```

```
entity Counter_TB is
end Counter_TB;
```

```
architecture Counter_TB_ARCH of Counter_TB is
```

```
-----TYPE DEFINITIONS-----
-- grouped expected outputs of Counter
type t_TEST is record
    digits: std_logic_vector(7 downto 0);
    mask: std_logic_vector(15 downto 0);
end record t_TEST;
```

```
-- a generic list of at least one test
type t_TEST_ARRAY is array (positive range <>) of t_TEST;
```

```
-----CONSTANTS-----
constant ACTIVE: std_logic := '1';

constant CLOCK_PERIOD: time := 10 ns;
constant STEP_TIME: time := 50 ns;
```

```
-- tests
constant ALL_TESTS: t_TEST_ARRAY(1 to 17) := (
    ( "00000000", "0000000000000001" ),
    ( "00000001", "0000000000000010" ),
    ( "00000010", "0000000000000100" ),
    ( "00000011", "0000000000001000" ),
    ( "00000100", "0000000000010000" ),
    ( "00000101", "0000000000100000" ),
    ( "00000110", "0000000001000000" ),
    ( "00000111", "0000000010000000" ),
    ( "00001000", "0000000100000000" ),
    ( "00001001", "0000001000000000" ),
    ( "00010000", "0000010000000000" ),
    ( "00010001", "0000100000000000" ),
    ( "00010010", "0001000000000000" ),
    ( "00010011", "0010000000000000" ),
    ( "00010100", "0100000000000000" ),
    ( "00010101", "1000000000000000" ),
    ( "00000000", "0000000000000001" )
);
```

```
-----COMPONENT-----
-- uut: counter
component Counter is
    port(
        clock: in std_logic;
        reset: in std_logic;

        countEn: in std_logic;

        digits: out std_logic_vector(7 downto 0); -- bcd tens (15:8), ones (7:0)
        mask: out std_logic_vector(15 downto 0)
    );
end component;
```



```

    );
end component;

-----FUNCTIONS-----
-- convert std_logic_vector to string for logging
function print_bits (
    bits: std_logic_vector
) return string is
    variable bitsString: string(1 to bits'length);
    variable i: integer range 1 to bits'length;
begin
    -- track position in string separately
    -- to show ranges in both directions correctly
    i = 1;

    -- set bits
    for j in bits'range loop
        -- note, std_logic'image takes the form "'X'", so extract 2nd char
        bitsString(i) := bitsString & std_logic'image(bits(j))(2);
        i := i + 1;
    end loop;

    -- return between quotes
    return "'" & bitsString & "'";
end function;

-----SIGNALS-----
signal clock: std_logic;
signal reset: std_logic;

signal countEn: std_logic;
signal digits: std_logic_vector(7 downto 0);
signal mask: std_logic_vector(15 downto 0);
begin
    DRIVE_RESET: process is
    begin
        reset <= ACTIVE;
        wait for 17 ns;

        reset <= not ACTIVE;
        wait;
    end process;

    DRIVE_CLOCK: process is
    begin
        clock <= not ACTIVE;
        wait for (CLOCK_PERIOD / 2);

        clock <= ACTIVE;
        wait for (CLOCK_PERIOD / 2);

        -- note, processes unterminated by a wait will repeat indefinitely
    end process;

    DRIVE_INPUTS: process is
    begin
        -- initialize signals
        countEn <= (not ACTIVE);

        -- wait until the first clock cycle after reset
        wait until (reset = not ACTIVE);
        wait until rising_edge(clock);

        -- wait a little longer
        wait for STEP_TIME;

        -- run all tests
        for i in ALL_TESTS'range loop
            -- alert if results do not match
            assert (digits = ALL_TESTS(i).digits)
                report "FAILED TEST #" & integer'image(i)
                & " (BCD). Expected " & print_bits(ALL_TESTS(i).digits)

```

```

        & ", received " & print_bits(digits);

    assert (mask = ALL_TESTS(i).mask)
        report "FAILED TEST #" & integer'image(i)
        & " (MASK). Expected " & print_bits(ALL_TESTS(i).mask)
        & ", received " & print_bits(mask);

    -- keep countEn active until next clock cycle to increment counter
    countEn <= ACTIVE;
    wait for CLOCK_PERIOD;

    -- keep countEn low for rest of step
    countEn <= (not ACTIVE);
    wait for (STEP_TIME - CLOCK_PERIOD);
end loop;

wait;
end process;

UUT: Counter port map(
    clock => clock,
    reset => reset,

    countEn => countEn,

    digits => digits,
    mask => mask
);
end Counter_TB_ARCH;

```